

SUB:-Hindi(Entire)

Resistivity (ρ)

$\rho = \text{rho.}$

Length

Area

Temperature.

$$R \propto l$$

$$R \propto \frac{1}{A}$$

$$R \propto \frac{l}{A}$$

$$R = k \times \frac{l}{A}$$

$$\boxed{k = \rho}$$

$$R = \rho \times \frac{l}{A}$$


$$\boxed{R = \frac{\rho l}{A}}$$

$$R \times A = \rho \times l$$

$$\boxed{\rho = \frac{RA}{l}}$$

SI unit of resistance = Ohm (Ω)

SI unit of resistivity = Ohm-metre ($\Omega\text{-m}$)

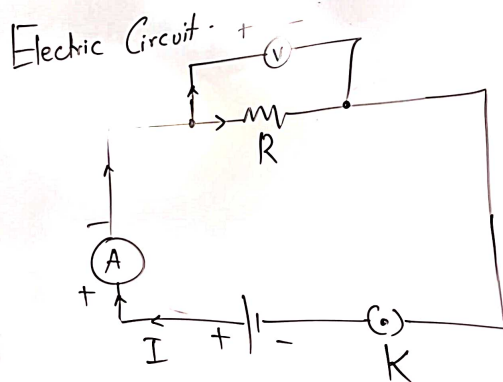SUB:-Hindi(Entire)

① Ammeter

- Used to measure current
- Connected in series.

② Voltmeter

- Used to measure potential difference.
- Connected in parallel.


SUB:-Hindi(Entire)

Components of electric circuit.

Symbol	Component	Symbol.
① Electric cell.	⑤ Connecting wires	⑨ Variable resistance.
② Battery.	⑥ Crossing wires.	⑩ Ammeter
③ Open tap key	⑦ Light bulb	⑪ Voltmeter
④ Closed tap key.	⑧ Resistance.	

SUB:-Hindi(Entire)

Resistors in series.

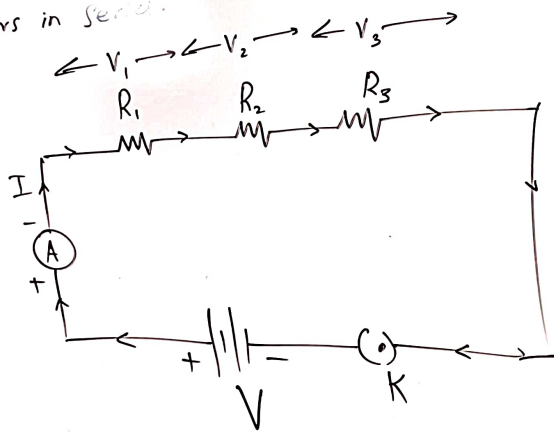

$$V = V_1 + V_2 + V_3 \quad \text{--- (1)}$$

By Ohm's Law,

$$\boxed{V = I \times R}$$

$$V = I \times R_s$$

$$V_1 = I \times R_1$$

$$V_2 = I \times R_2$$

$$V_3 = I \times R_3$$

--- (2)

Put above values in eq. (1)

$$I R_s = I R_1 + I R_2 + I R_3$$

$$\cancel{I} R_s = \cancel{I} (R_1 + R_2 + R_3)$$

$$\boxed{R_s = R_1 + R_2 + R_3}$$

For n resistors.

$$\boxed{R_s = R_1 + R_2 + \dots + R_n}$$


R_s = effective series resistance

$$R_1 = 10 \Omega, R_2 = 10 \Omega \\ R_3 = 10 \Omega$$

$$R_s = R_1 + R_2 + R_3 \\ = 10 + 10 + 10$$

$$\boxed{R_s = 30 \Omega}$$

SUB:-Hindi(Entire)

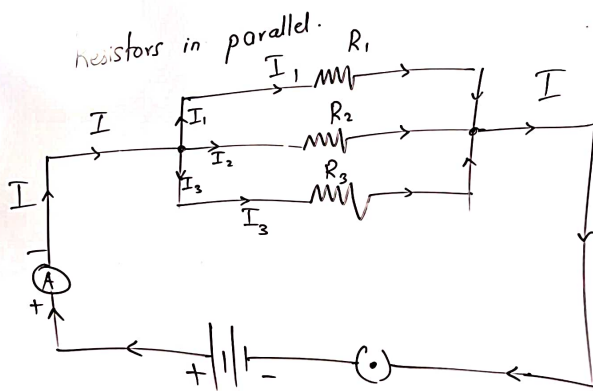

$$I = I_1 + I_2 + I_3 \quad \text{--- ①}$$

By Ohm's Law.

$$V = I \times R$$

$$\left. \begin{aligned} I &= \frac{V}{R} \\ I &= \frac{V}{R_p} \\ I_1 &= \frac{V}{R_1} \\ I_2 &= \frac{V}{R_2} \\ I_3 &= \frac{V}{R_3} \end{aligned} \right\} \quad \text{--- ②}$$

Put above values in eq. ①

$$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{V}{R_p} = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

R_p = effective parallel resistance.

For n resistors

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

If $R_1 = R_2 = R_3 = 10 \Omega$

$$\frac{1}{R_p} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10}$$

$$\frac{1}{R_p} = \frac{3}{10}$$

$$R_p = \frac{10}{3}$$

$$R_p = 3.33 \Omega$$

9/8/2021

Friday

Learn something new today.

Q a) (given): $l_1 = 1\text{ m} = 100\text{ cm}$

$$R_1 = 6\ \Omega$$

$$l_2 = 70\text{ cm}$$

To find: $R_2 = ?$ Solution: $R \propto l$

$$R = k \times l$$

$$R_1 = k \times l_1 \quad \text{--- ①}$$

$$R_2 = k \times l_2 \quad \text{--- ②}$$

Divide eq ② by ①

$$\frac{R_2}{R_1} = \frac{k \times l_2}{k \times l_1}$$

$$\frac{R_2}{R_1} = \frac{l_2}{l_1}$$

$$\frac{R_2}{6} = \frac{70}{100}$$

$$R_2 = \frac{70 \times 6}{100}$$

$$R_2 = \frac{420}{100} = 4.2\ \Omega$$

4/8/2021
Friday

Learn something new today.

Given $R_p = 80 \Omega$
 $R_p = 20 \Omega$

To find: $R_1 = ?$
 $R_2 = ?$

Solution: $R_s = 80 \Omega$
 $R_1 + R_2 = 80 \quad \text{--- (1)}$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{20} = \frac{R_2 + R_1}{R_1 \times R_2}$$

$$\frac{1}{20} \times \frac{80}{R_1 \times R_2} \quad \text{(From 1)}$$

$$R_1 \times R_2 = 1600$$

$$\boxed{R_2 = \frac{1600}{R_1}} \quad \text{--- (2)}$$

$$R_1 + R_2 = 80 \quad \text{(From 1)}$$

$$R_1 + \frac{1600}{R_1} = 80 \quad \text{(From 2)}$$

Multiply throughout by R_1

$$R_1 \times R_1 + R_1 \times \frac{1600}{R_1} = 80 \times R_1$$

$$R_1^2 + 1600 = 80R_1$$

$$R_1^2 - 80R_1 + 1600 = 0$$

$$R_1 \times R_1 - 40R_1 - 40R_1 + 40 \times 40 = 0$$

$$R_1(R_1 - 40) - 40(R_1 - 40) = 0$$

$$(R_1 - 40)(R_1 - 40) = 0$$

$$R_1 - 40 = 0 \quad \text{or} \quad R_1 - 40 = 0$$

$$R_1 = 40 \quad \text{or} \quad R_1 = 40$$

$$\boxed{R_1 = 40 \Omega}$$

$$R_1 + R_2 = 80$$

$$40 + R_2 = 80$$

$$R_2 = 80 - 40$$

$$\boxed{R_2 = 40 \Omega}$$

4/8/2024
Friday

Learn something new today

c)

$$Q = 4200$$
$$t = 5 \text{ min} = (5 \times 60) \text{ s}$$

To find: $I = ?$

Solution: $I = \frac{Q}{t}$

$$= \frac{4200}{5 \times 60} = \frac{7}{5}$$

$$\boxed{I = 1.4 \text{ A}}$$

$$\begin{array}{r} 1.4 \\ 5 \overline{) 7} \\ \underline{-5} \\ 20 \\ \underline{-20} \\ 0 \end{array}$$

20/8/24

Tuesday

Refractive Index (n)

① $n = \frac{\sin i}{\sin r}$

② Refractive index of first medium w.r.t second medium

$\rightarrow {}_1n_2 = \frac{v_2}{v_1}$

$\rightarrow {}_1n_2 = \frac{\rho_2}{\rho_1}$

Refractive index of second medium w.r.t first medium

$\rightarrow {}_2n_1 = \frac{v_1}{v_2}$

$\rightarrow {}_2n_1 = \frac{n_2}{n_1}$

